

Homework 8


①

7.33) At any given time the flux is $\boxed{\Phi = \pi a^2 B}$

If B changes, then Φ changes, therefore there is an emf. In magnitude $\boxed{\text{emf} = \frac{d\Phi}{dt}}$

If the ring was a conductor, we would get current flowing. But the ring is an insulator, so current does not flow. However, there is an $\vec{E}$ field associated with the emf inside the ring. Since the ring is charged, this $\vec{E}$ field will cause a force, and this force will cause a torque. Why a torque?

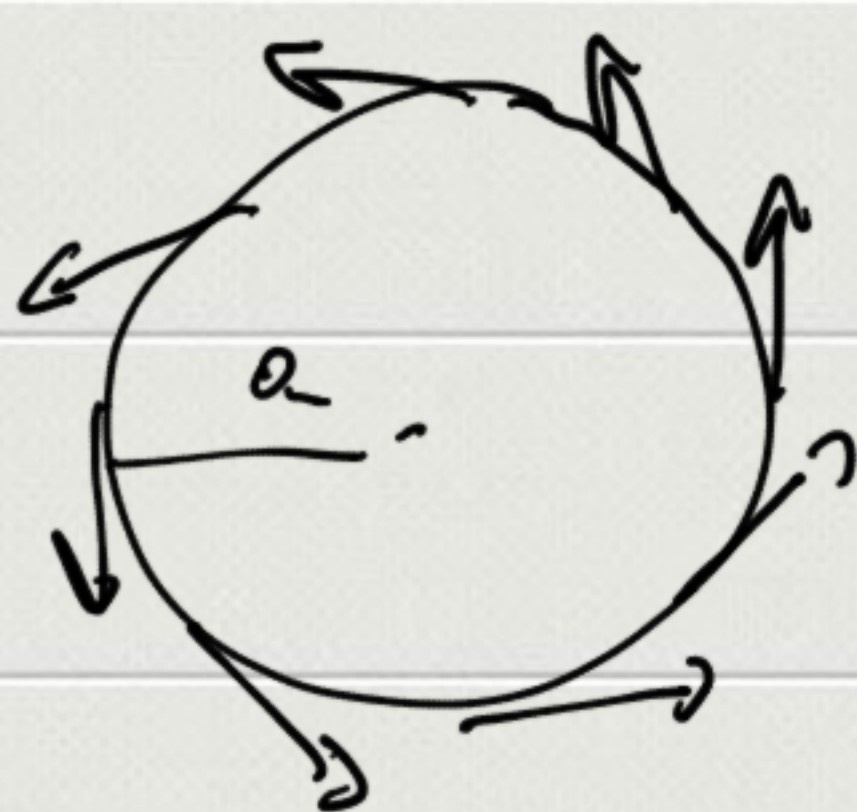Because the forces on each charge element are tangential:



I will not bother keeping track of signs —

$\tau = F a = q E a$ — Now we need to find E .

$$\text{emf} = \frac{d\Phi}{dt} \quad \text{but} \quad \text{emf} = \int \vec{E} \cdot d\vec{l} = 2\pi a E$$

$$2\pi a E(t) = \pi a^2 \frac{dB}{dt} \quad E(t) = \frac{1}{2} a \frac{dB}{dt}$$

$$\rightarrow \tau(t) = \frac{1}{2} q^2 a \frac{dB}{dt}$$

Let L = angular momentum $L = I\omega$, where I is the moment of inertia.

We have $\tau = \frac{dL}{dt} = \pm \frac{dw}{dt}$

(2)

$$\frac{1}{2} q a^2 \frac{dB}{dt} = I \frac{dw}{dt} = m a^2 \frac{dw}{dt} \quad (I = m a^2)$$

$$\frac{dw}{dt} = \frac{q}{2m} \frac{dB}{dt}$$

Integrate w from $0 \rightarrow w$
Integrate B from $B_0 \rightarrow 0$

Up to a sign, I then get $\boxed{w = \frac{q B_0}{2m}}$

7.36 (a) If I_2 increases, there will be extra flux through the top circuit pointing up. Therefore the induced emf in the top circuit must make an extra downward flux. The induced current must then be negative $\Rightarrow \mathcal{E}_1 = -L_1 \frac{dI_1}{dt} - M \frac{dI_2}{dt}$ (1)

Exact same argument leads to

$$\mathcal{E}_2 = -L_2 \frac{dI_2}{dt} - M \frac{dI_1}{dt} \quad (2)$$

If we were to switch the convention for the I_2 and +ve $\mathcal{E}_2$, we would get the opposite sign, ie, $+M dI/dt$

Figure (b)

(b) Key idea here is that in this case $I_1 = I_2 = I$

Also the total emf $\mathcal{E}$ is $\mathcal{E}_1 + \mathcal{E}_2$

Then adding equations (1) and (2) above,

I get $\mathcal{E} = -(L_1 + L_2 + 2M) \frac{dI}{dt} \Rightarrow \boxed{L' = L_1 + L_2 + 2M}$


if instead we connect the coils like ③
 in figure (c) $I_1 = -I_2$ - Write $I = I_1$
 Then $\text{emf} = \mathcal{E}_1 - \mathcal{E}_2$ - Subtract off
 equations (1) and (2) - This gives

$$\mathcal{E} = \mathcal{E}_1 - \mathcal{E}_2 = -L_1 \frac{dI}{dt} - M \frac{d(-I)}{dt} + L_2 \frac{d(-I)}{dt} + M \frac{dI}{dt}$$

$$\mathcal{E} = -(L_1 + L_2 - 2M) \frac{dI}{dt} \quad \boxed{L'' = L_1 + L_2 - 2M}$$

(c) Since $L'' \geq 0$, must have $\boxed{M \leq \frac{L_1 + L_2}{2}}$

7.41

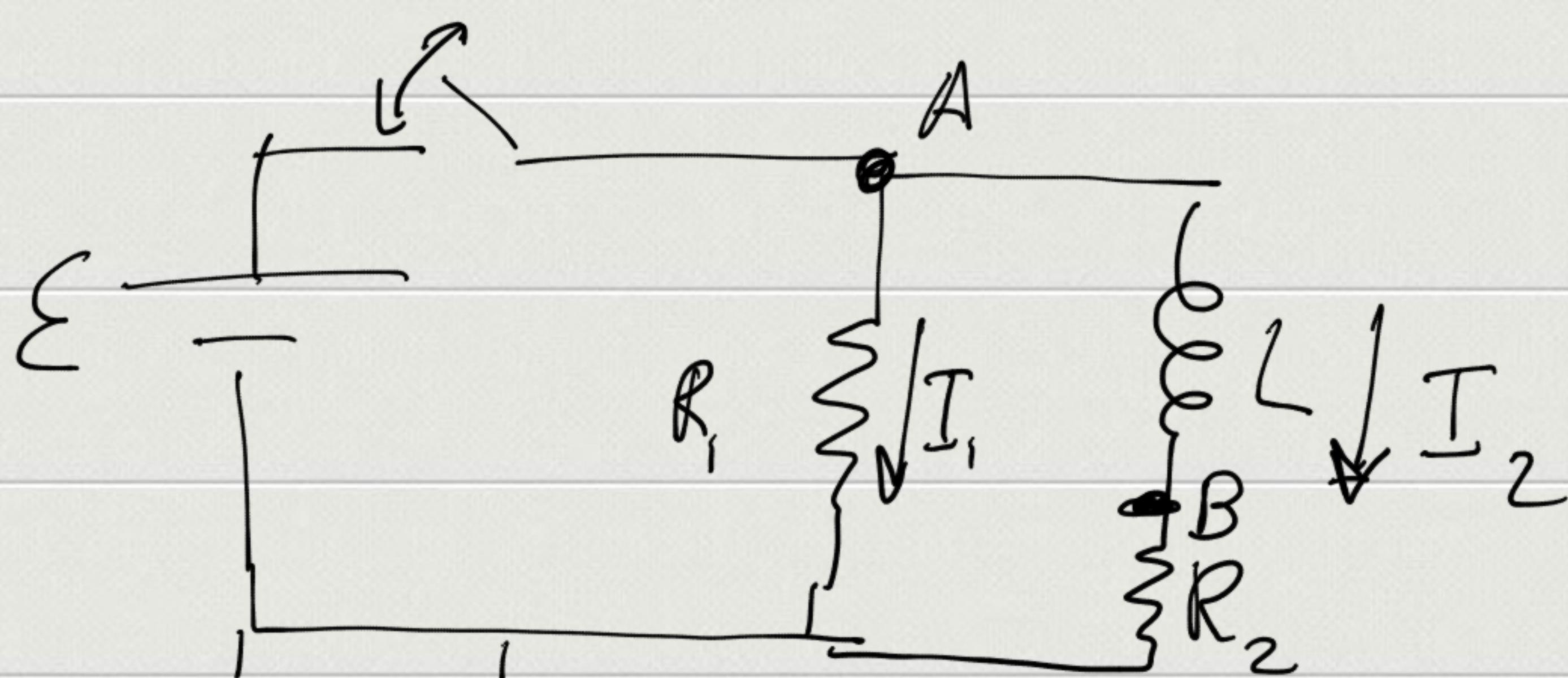

$$\mathcal{E} = 10\text{V} \quad R_1 = 150\Omega \quad R_2 = 50\Omega \quad L = 0.1\text{H}$$

When the switch has been closed for a long time, all transients have died out -

$$\text{Thus } V_A = \mathcal{E} = 10\text{V} \quad V_B = V_A = 10\text{V}$$

$$I_1 = V_A / R_1 = 0.067\text{A} \quad \underline{\underline{\quad \quad \quad}}$$


$$I_2 = \frac{V_B}{R_2} = \frac{V_A}{R_2} = 0.20\text{A}$$

When we open the switch, the circuit now looks like this (4)

$$V_A - V_B = L \frac{dI}{dt} \quad (1)$$

$$V_B - V_C = V_B = I R_2 \quad (2)$$

$$V_C - V_A = -V_A = I R_1 \quad (3)$$

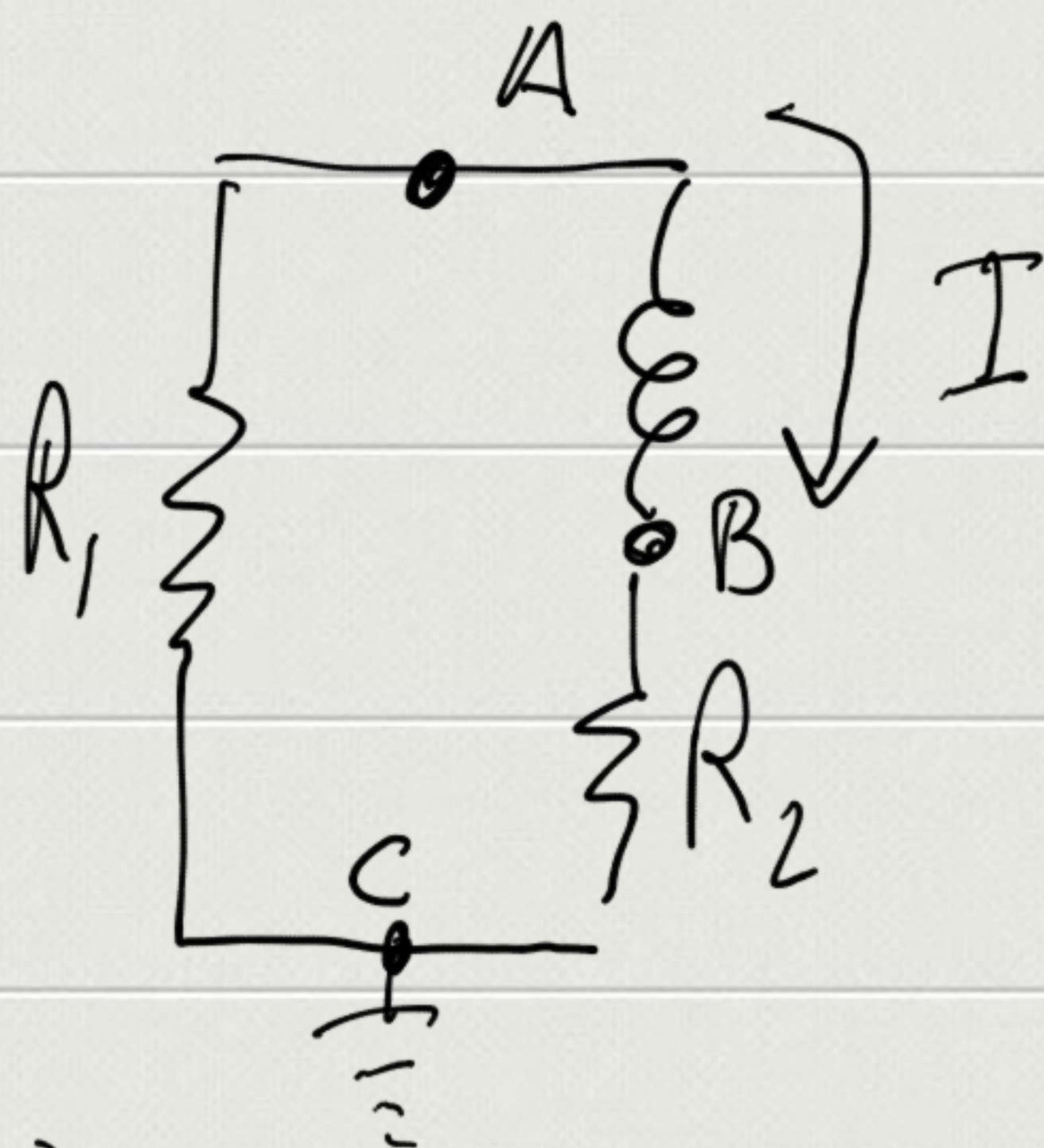

$$\underline{V_C = 0}$$

$$L \frac{dI}{dt} + I(R_1 + R_2) = 0$$

Assuming that the switch is closed at $t=0$, the solution is $I = I_0 e^{-t/\tau}$


$$\text{with } \tau = L/R_1 + R_2 = 0.1/200 \text{ sec} = \underline{0.5 \text{ msec}}$$

I_0 is given by the value from the previous page

i.e. $I_0 = 0.2 \text{ A}$ - Then from eqns 2 & 3 we can get V_A and V_B as a function of time.


$$V_B = I R_2 = 10 \text{ V } e^{-t/\tau}$$
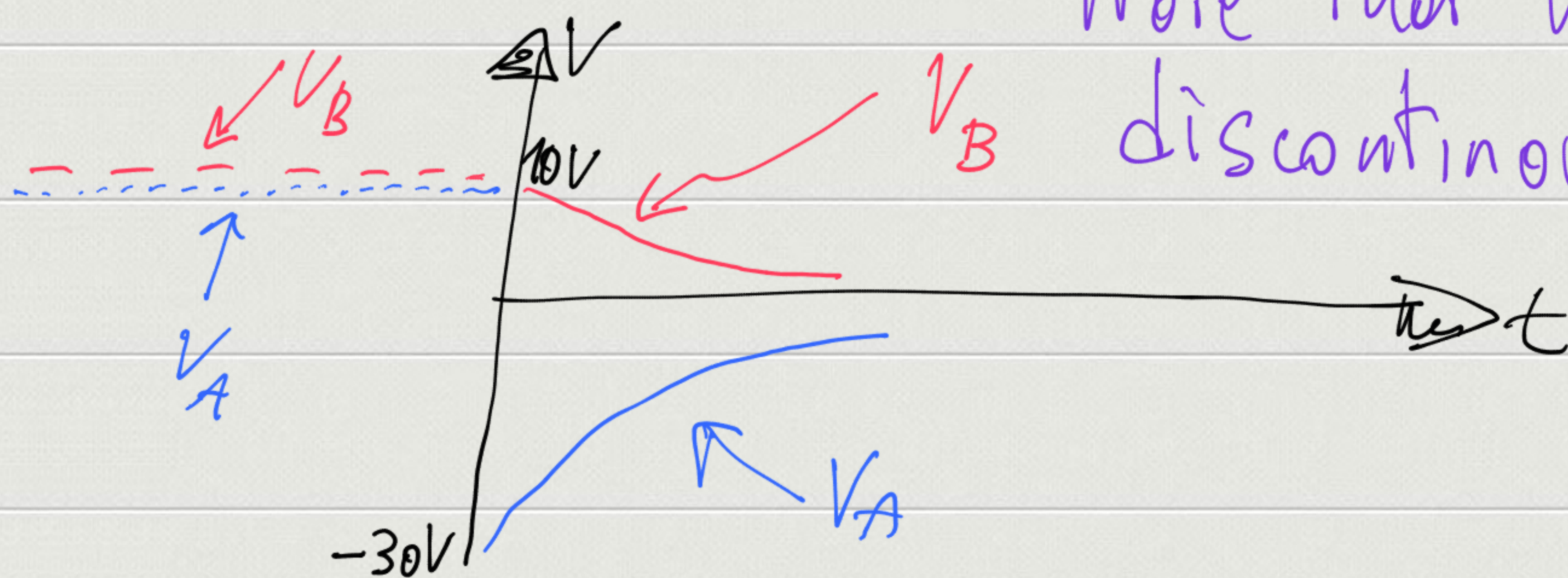
$$V_A = -I R_1 = -30 \text{ V } e^{-t/\tau}$$



Note that V_A is discontinuous!!

7.42

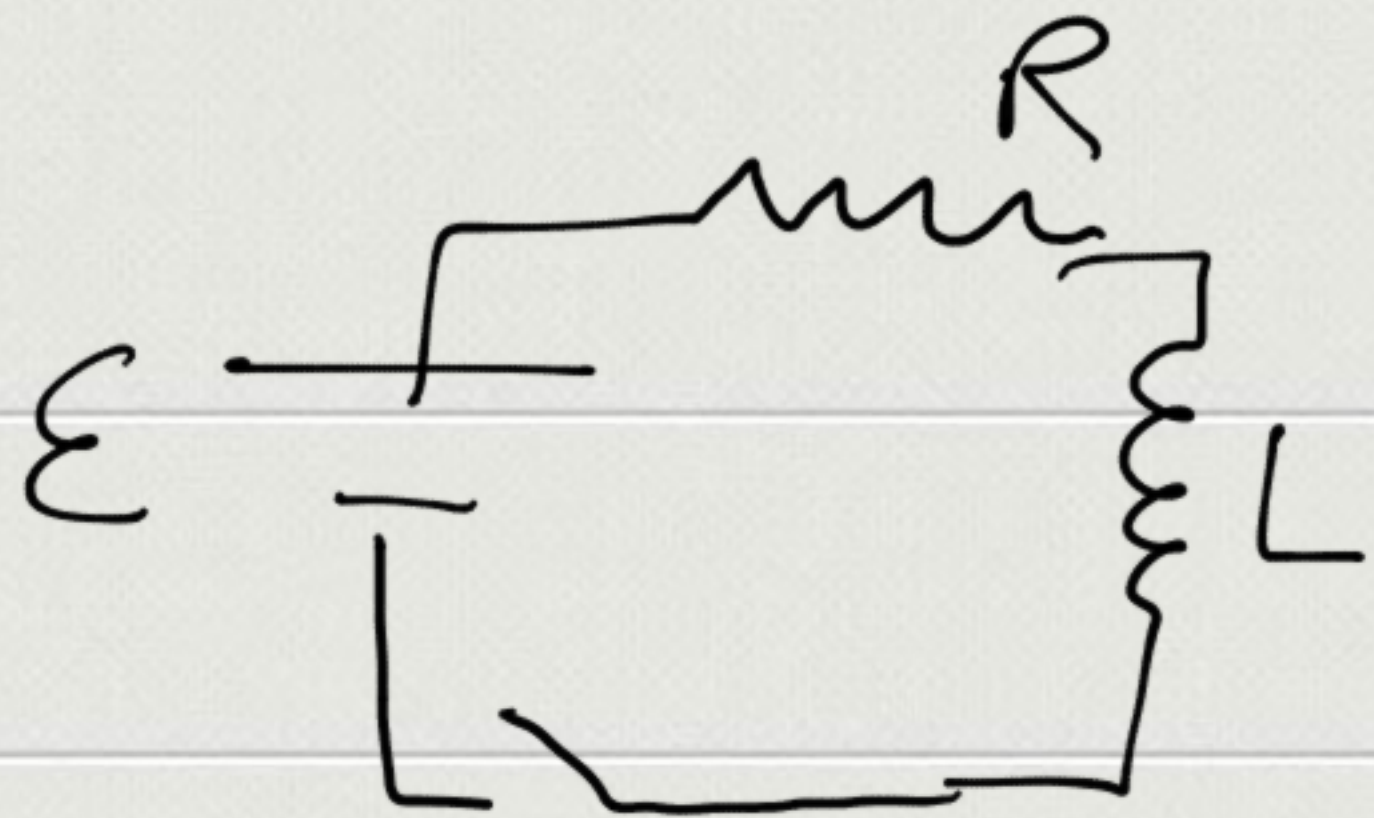

$$\begin{aligned}\mathcal{E} &= 12\text{V} \\ R &= 0.01\Omega \\ L &= 5 \cdot 10^{-4}\text{H}\end{aligned}$$

5

$$I = I_0(1 - e^{-t/\tau}) \quad \tau = L/R \quad I_0 = \frac{\mathcal{E}}{R}$$

$$\text{Want } e^{-t/\tau} = 0.1 \quad \frac{t}{\tau} = \log 10$$

$$t = \log 10 \cdot \frac{L}{R} = \underline{\underline{0.115 \text{ sec}}}$$

$$E = \frac{1}{2} L I^2 = \frac{1}{2} L \left(\frac{9}{10} I_0 \right)^2 = \frac{81}{200} L \frac{\mathcal{E}^2}{R^2}$$

$$E = \frac{81}{200} 5 \cdot 10^{-4} \frac{12^2}{10^{-4}} \text{ J} = \underline{\underline{292 \text{ J}}}$$

For the energy delivered by the battery, we cannot simply answer "292 J" because there have been $I^2 R$ losses in the resistor. (Remember: $I^2 R$ is power, ie, dE/dt). We can do this two ways. (a) integrate $I^2 R$ and add it to 292 J; or (b) integrate $\mathcal{E} I$, which is the power instantaneously delivered by the battery. Let's do it both ways

$$E = \int_0^{t_1} \varepsilon_0 I dt \quad t_1 = \log 10 \frac{L}{R} \quad (6)$$

$$E = \varepsilon_0 I_0 \int_0^{t_1} (1 - e^{-t/\tau}) dt = \varepsilon_0 I_0 \left[t_1 + \tau e^{-t_1/\tau} - \tau \right]$$

Note: $e^{-t_1/\tau} = \frac{1}{10}$

$$E = \varepsilon_0 I_0 \left[t_1 - \frac{9}{10} \tau \right] = \frac{\varepsilon_0^2 L}{R^2} \left[\log 10 - \frac{9}{10} \right]$$

$$E = \frac{12^2 \cdot 5 \cdot 10^{-4}}{10^{-4}} \left[\log 10 - \frac{9}{10} \right] = \underline{\underline{1010 \text{ J}}}$$

This means that $1010 \text{ J} - 292 \text{ J} = \underline{\underline{718 \text{ J}}}$ must have been dissipated in the resistor.

Let's verify that

$$E_{\text{resistor}} = \int I^2 R dt = I_0^2 R \int_0^{t_1} (1 - e^{-t/\tau})^2 dt$$


$$= \frac{\varepsilon_0^2}{R} \int_0^{t_1} (1 - 2e^{-t/\tau} + e^{-2t/\tau}) dt =$$

$$= \frac{\varepsilon_0^2}{R} \left[t_1 + 2\tau e^{-t_1/\tau} - \tau - \frac{\tau}{2} e^{-2t_1/\tau} + \frac{\tau}{2} \right]$$

$$= \frac{\varepsilon_0^2}{R} \left[t_1 - 2 \cdot \frac{9}{10} \tau + \frac{1}{2} \frac{99}{100} \tau \right] = \frac{\varepsilon_0^2 L}{R^2} \left[\log 10 - \frac{18}{10} + \frac{99}{200} \right]$$

$$= \frac{12^2 \cdot 5 \cdot 10^{-4}}{10^{-4}} [0.997] = \underline{\underline{718 \text{ J}}} \quad \checkmark \quad \underline{\underline{\text{Yes!!}}}$$

8.16

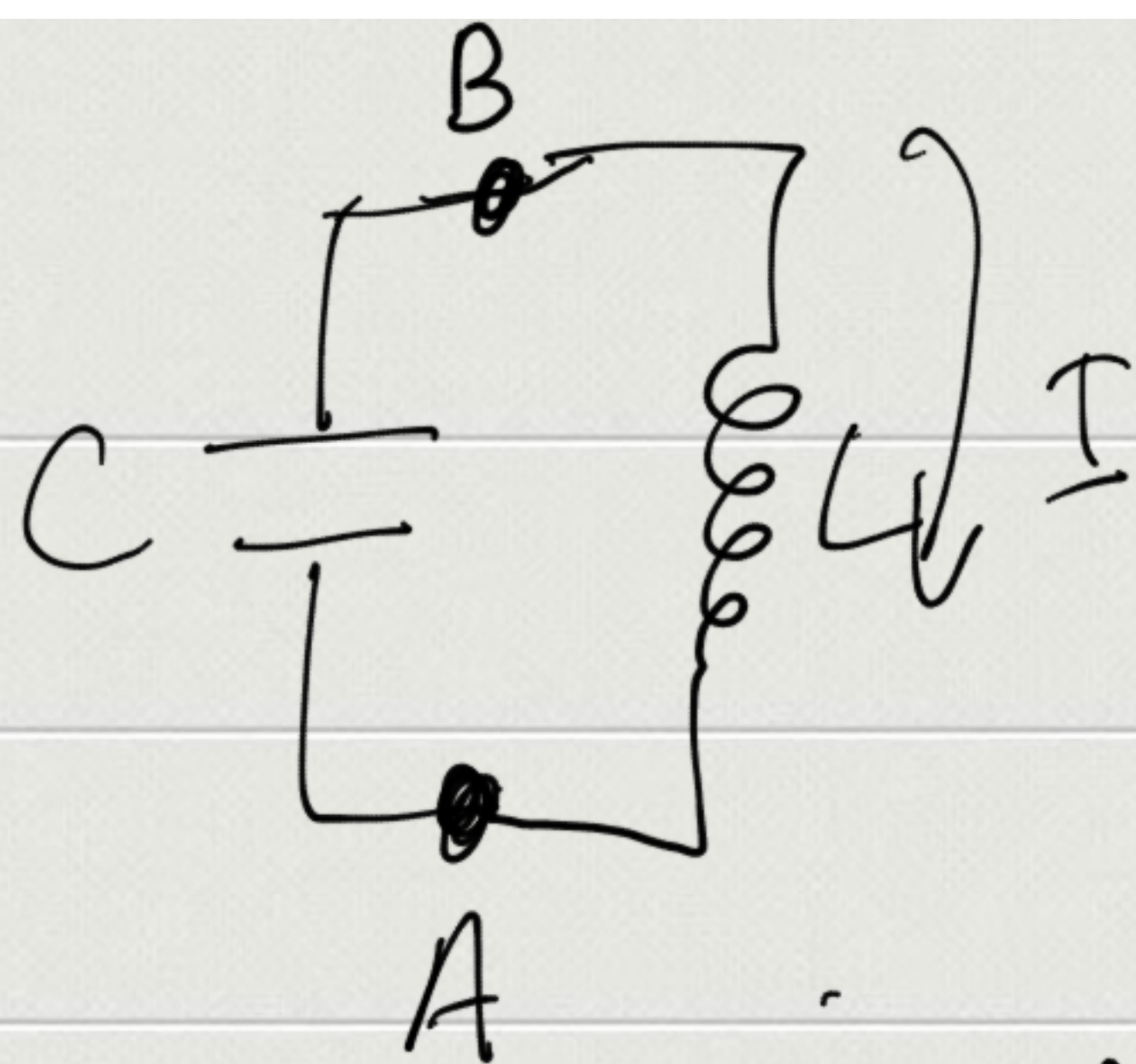

(7)

$$V_A - V_B = V_0 \cos \omega t \quad (\text{voltage across } C)$$

$$V_B - V_C = -V_0 \cos \omega t \quad (\text{voltage across } L)$$

$$\text{Current } L \frac{dI}{dt} = -V_0 \cos \omega t \Rightarrow I = -\frac{V_0}{\omega L} \sin \omega t$$

$$\text{or } I = V_0 \sqrt{\frac{C}{L}} \sin \omega t$$

$$\text{Energy in the inductor } U_L = \frac{1}{2} L I^2 = \frac{1}{2} V_0^2 C \sin^2 \omega t$$

$$\text{Energy in the capacitor } U_C = \frac{1}{2} C (V_A - V_B)^2 = \frac{1}{2} V_0^2 C \cos^2 \omega t$$


$$\text{Note: } U_L + U_C = \frac{1}{2} C V_0^2 \text{ is constant}$$

At $t=0$


$$U_L = 0 \quad U_C = \frac{1}{2} C V_0^2$$

At $t = \frac{\pi}{2\omega}$
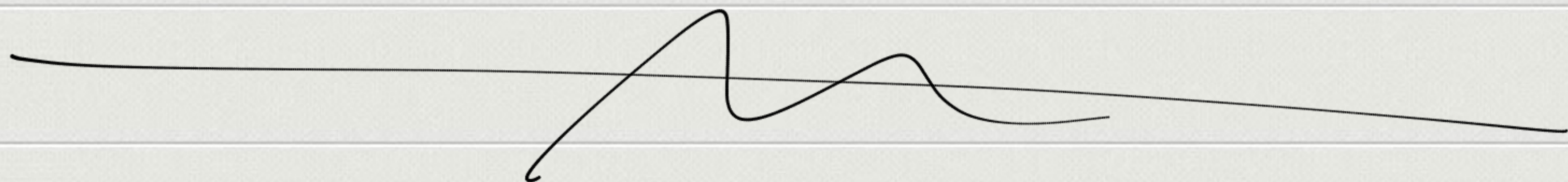
$$U_L = \frac{1}{2} C V_0^2 \quad U_C = 0$$



8.24

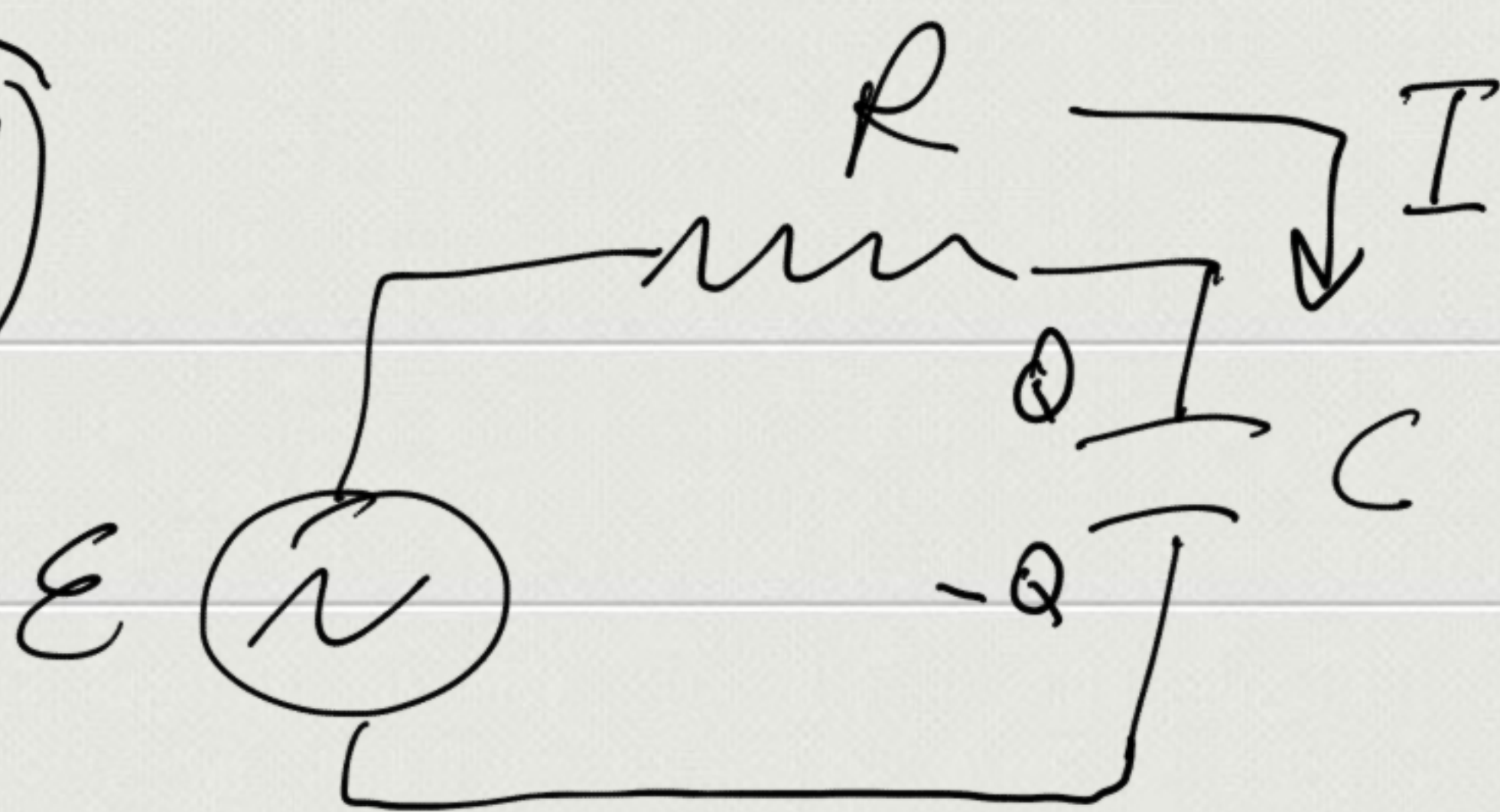

8

$$IR + \frac{Q}{C} = \varepsilon_0 \cos \omega t$$

$$R \frac{dQ}{dt} + \frac{Q}{C} = \varepsilon_0 \cos \omega t = \varepsilon_0 e^{i\omega t}$$

Write $Q = \tilde{Q}_0 e^{i\omega t} \Rightarrow \frac{dQ}{dt} = i\omega \tilde{Q}_0 e^{i\omega t}$

$$i\omega R \tilde{Q}_0 + \frac{\tilde{Q}_0}{C} = \varepsilon_0 \quad \tilde{Q}_0 = \frac{C \varepsilon_0}{1 + i\omega RC}$$

But we wanted current, so $I = \tilde{I}_0 e^{i\omega t}$

$$\text{and } \tilde{I}_0 = i\omega \tilde{Q}_0 = \frac{i\omega C \varepsilon_0}{1 + i\omega RC} = \frac{i\omega C \varepsilon_0 (1 - i\omega RC)}{1 + \omega^2 R^2 C^2}$$

$$\tilde{I}_0 = \frac{\varepsilon_0 \omega^2 R C^2 + i \varepsilon_0 \omega C}{1 + \omega^2 R^2 C^2}$$

Now write $\tilde{I}_0 = I_0 e^{i\phi}$

$$\tan \phi = \frac{\varepsilon_0 \omega C}{\varepsilon_0 \omega^2 R C^2} = \frac{1}{\omega RC}$$

$$I_0 = \frac{\varepsilon_0 \sqrt{\omega^4 R^2 C^4 + \omega^2 C^2}}{1 + \omega^2 R^2 C^2} = \frac{\varepsilon_0 \omega C \sqrt{1 + \omega^2 R^2 C^2}}{1 + \omega^2 R^2 C^2}$$

$$I_0 = \frac{\omega C E_0}{\sqrt{1 + \omega^2 R^2 C^2}} = \frac{E_0}{\sqrt{R^2 + 1/\omega^2 C^2}}$$

(9)

Now take the real part of $\tilde{I} e^{i\omega t} = I_0 e^{i(\omega t + \phi)}$

$$I(t) = \frac{E_0}{\sqrt{R^2 + 1/\omega^2 C^2}} \cos(\omega t + \phi)$$

with $\phi = \tan^{-1} \frac{1}{R\omega C}$

For large ω , amplitude $\Rightarrow E_0/R$
 phase $\Rightarrow 0$

This makes sense, because at high ω the capacitor is 'like a short'

For small ω , the amplitude goes to zero. This makes sense because for DC currents the capacitor does not conduct