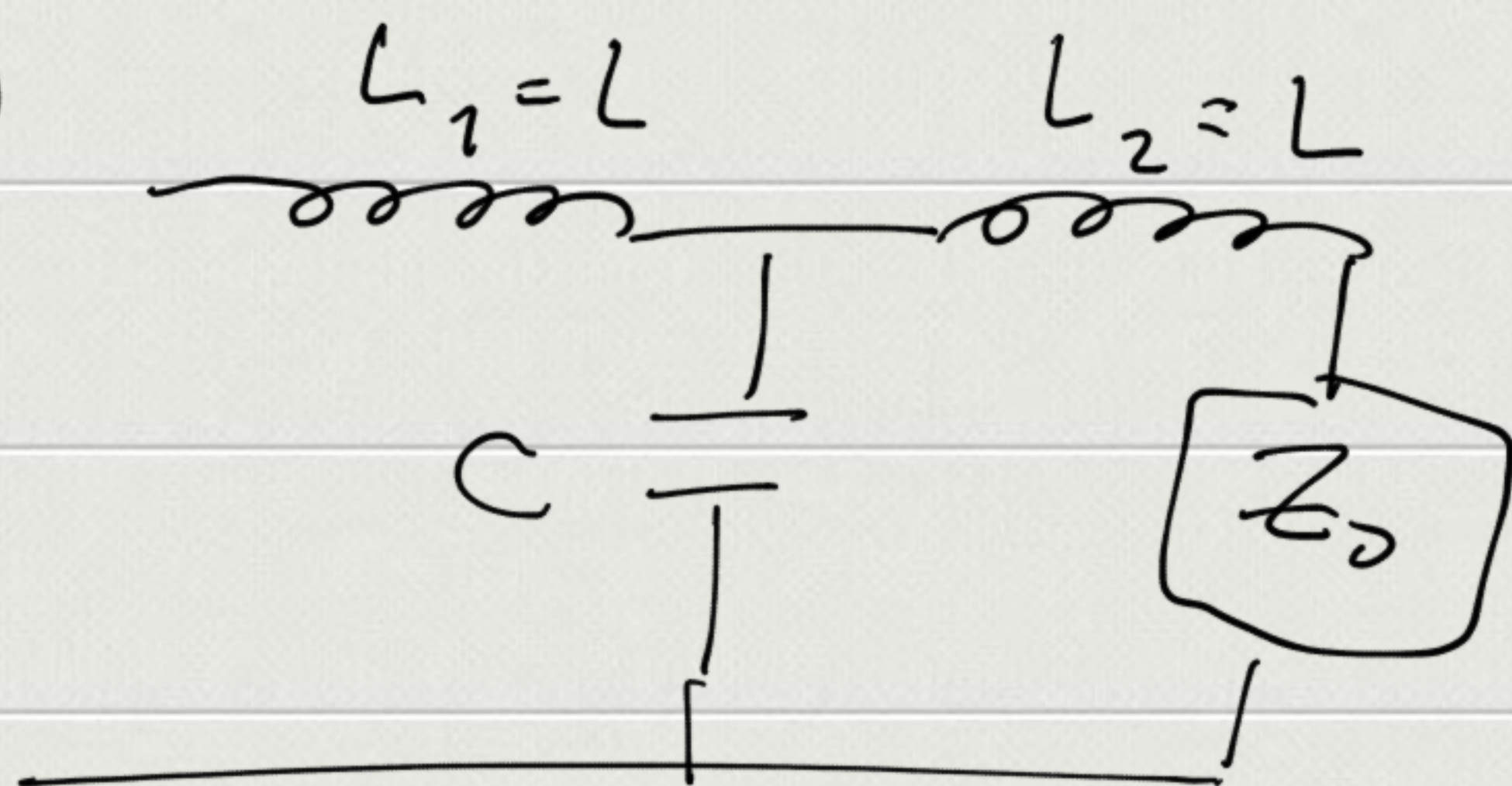



HOMEWORK 9

1

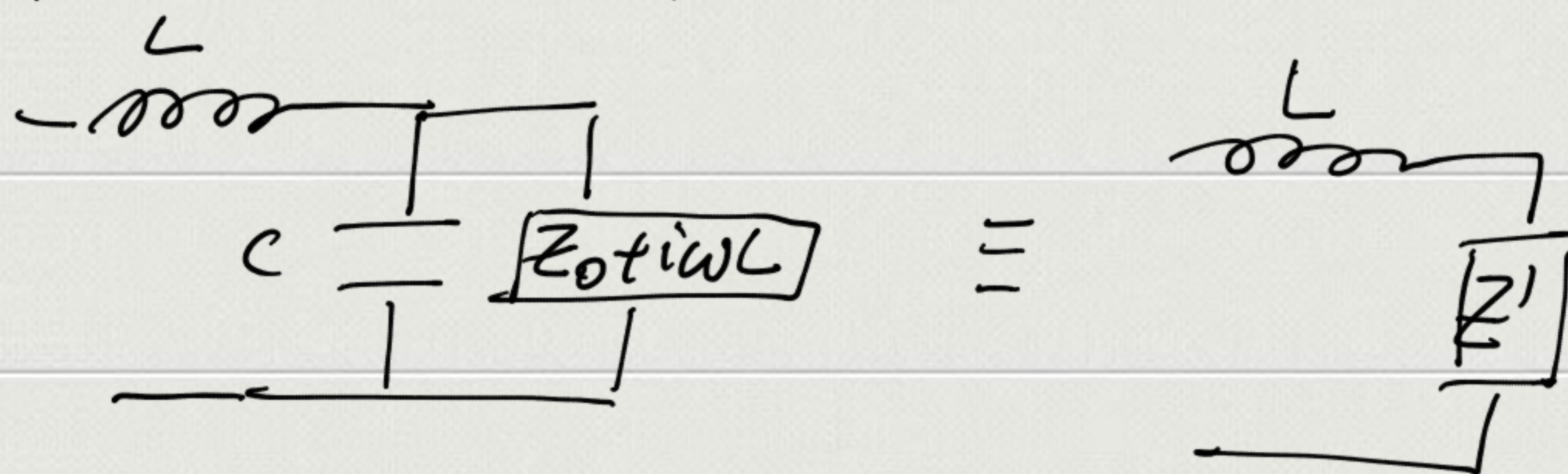8.34



L_2 and Z_0 are in series. Their total impedance is $Z_0 + i\omega L$. Then this new impedance is in parallel with C .



$$\text{with } \frac{1}{Z'} = \frac{1}{Z_0 + i\omega L} + i\omega C = \frac{1 + i\omega C Z_0 - \omega^2 LC}{Z_0 + i\omega L}$$

$$Z' = \frac{Z_0 + i\omega L}{1 + i\omega C Z_0 - \omega^2 LC}$$

Then, Z' is in series with L . So the total impedance is $Z = Z' + i\omega L$

$$Z = \frac{Z_0 + i\omega L}{1 - \omega^2 LC + i\omega C Z_0} + i\omega L$$

We want $Z = Z_0$, therefore

$$\frac{Z_0 + i\omega L}{1 - \omega^2 LC + i\omega C Z_0} + i\omega L = Z_0$$

$$Z_0 + i\omega L + i\omega L - i\omega^3 L^2 C - \omega^2 LC Z_0 = Z_0 - \omega^2 LC Z_0 + i\omega C Z_0^2$$

$$2i\omega L - i\omega^3 L^2 C = i\omega C Z_0^2$$

$$2L - \omega^2 L^2 C = C Z_0^2$$

$$Z_0 = \sqrt{\frac{2L - \omega^2 L^2 C}{C}}$$

This is a pure resistance if the argument of the square root is positive, i.e.,

$$2L - \omega^2 L^2 C > 0 \quad 2 > \omega^2 L C$$

$$\omega^2 < \frac{2}{LC}$$

$$\text{At } \omega^2 = \frac{2}{LC}, \quad Z_0 = 0$$

8.38

We have R and C in series, and then
(a) the combination in parallel with R

$$R \& C \text{ in series: } Z' = R + \frac{1}{i\omega C} = \frac{1 + i\omega CR}{i\omega C}$$

$$\text{But } \omega RC = 1 \text{ and } \omega C = \frac{1}{R} \Rightarrow Z' = R \frac{(1+i)}{i} = R(1-i)$$

Then, Z' in parallel with R gives

$$\frac{1}{Z} = \frac{1}{Z'} + \frac{1}{R} = \frac{1}{R} \left(\frac{1}{1-i} + 1 \right) = \frac{1}{R} \frac{2-i}{1-i}$$

$$\Rightarrow Z = R \frac{1-i}{2-i} \quad \text{or} \quad Z = R \frac{(1-i)(2+i)}{5}$$

$$Z = \frac{R}{5} (3-i)$$

$$(b) \mathcal{E} = \mathcal{E}_0 e^{i\omega t}$$

(3)

$$\underline{I} = \frac{\mathcal{E}}{Z} = \frac{\mathcal{E}_0 e^{i\omega t}}{R(\frac{1}{5})(3-i)} = \frac{5\mathcal{E}_0}{R} e^{i\omega t} \frac{1}{3-i}$$

Let's write $\frac{1}{3-i}$ as $A e^{i\phi}$

$$\frac{1}{3-i} = \frac{3+i}{10} \quad A^2 = \sqrt{\left(\frac{3}{10}\right)^2 + \left(\frac{1}{10}\right)^2} = \frac{1}{\sqrt{10}}$$

$$\boxed{\phi = \tan^{-1} \frac{1}{3}}$$

$$\text{Then } \underline{I} = \frac{5\mathcal{E}_0}{R} \frac{1}{\sqrt{10}} e^{i(\omega t + \phi)} = \frac{5\sqrt{10}}{10} \frac{\mathcal{E}_0}{R} e^{i(\omega t + \phi)}$$

$$\text{Writing } I = I_0 \cos(\omega t + \phi) = I_0 \operatorname{Re}[e^{i(\omega t + \phi)}]$$

$$\text{we get } \boxed{I_0 = \frac{5\sqrt{10}}{10} \frac{\mathcal{E}_0}{R} = \frac{\sqrt{10}}{2} \frac{\mathcal{E}_0}{R}}$$

$$(c) \text{ Average power } \langle P \rangle = I_0 \mathcal{E}_0 \frac{\cos \phi}{2}$$

$$\langle P \rangle = \frac{\sqrt{10}}{4} \frac{\mathcal{E}_0^2}{R} \cos \phi \quad \text{We know } \tan \phi = \frac{1}{3}$$

$$\frac{\sin \phi}{\cos \phi} = \frac{1}{3} \quad \sin \phi = \frac{1}{3} \cos \phi \quad \sin^2 \phi = \frac{1}{9} \cos^2 \phi$$

$$1 - \cos^2 \phi = \frac{1}{9} \cos^2 \phi \quad \cos^2 \phi = \frac{9}{10} \quad \cos \phi = \frac{3}{\sqrt{10}}$$

$$\Rightarrow \langle P \rangle = \frac{\sqrt{10}}{4} \frac{\mathcal{E}_0^2}{R} \frac{3}{\sqrt{10}} \quad \boxed{\langle P \rangle = \frac{3\mathcal{E}_0^2}{4R}}$$

(4)

Q.15 $E = \frac{\sigma}{\epsilon_0} = \frac{Q}{\pi b^2 \epsilon_0}$

$\frac{\partial \vec{E}}{\partial t} = \frac{1}{\pi b^2 \epsilon_0} \frac{\partial Q}{\partial t} = \frac{1}{\pi b^2 \epsilon_0} I$ ← Field inside capacitor

Using the paths suggested in the problem

$$\int_C \vec{B} \cdot d\vec{s} = \int_S \mu_0 \epsilon_0 \frac{\partial \vec{E}}{\partial t} \cdot d\vec{A}$$

$$B(r) 2\pi r = \mu_0 \epsilon_0 \frac{1}{\pi b^2 \epsilon_0} I \pi r^2$$

$$B(r) = \frac{\mu_0 I r}{2\pi b^2}$$

Q.18 Let $k = \frac{2\pi}{\lambda}$

$$\vec{E} = E_0 (\hat{x} + \hat{y}) \sin k(z + ct)$$

$$\vec{\nabla} \times \vec{E} = - \frac{\partial \vec{B}}{\partial t} \quad \text{and} \quad \text{curl } \vec{B} = \frac{1}{c^2} \frac{\partial \vec{E}}{\partial t}$$

$$\vec{\nabla} \times \vec{E} = \begin{vmatrix} \hat{x} & \hat{y} & \hat{z} \\ \frac{\partial}{\partial x} & \frac{\partial}{\partial y} & \frac{\partial}{\partial z} \\ E_0 \sin k(z+ct) & E_0 \sin k(z+ct) & 0 \end{vmatrix} =$$

$$\vec{\nabla} \times \vec{E} = + E_0 k \cos k[z+ct] (-\hat{x} + \hat{y}) \quad (5)$$

and this is $= - \frac{\partial \vec{B}}{\partial t}$

Therefore $\vec{B} = \frac{E_0}{c} \sin k[z+ct] (\hat{x} - \hat{y})$

Note $\vec{E} \perp \vec{B}$!!

9.25 $U = E_0 \langle E^2 \rangle = 4 \cdot 10^{-14} \frac{J}{m^3}$

Since $\epsilon_0 = 8.85 \cdot 10^{-12} \frac{C^2}{Kg m^3}$

$\langle E^2 \rangle = 4.5 \cdot 10^{-3} \frac{V^2}{m^2}$

$E_{rms} = \sqrt{\langle E^2 \rangle} = 0.07 \frac{V}{m}$

Assume that the kW radiated by the radio transmitter is radiated uniformly in space (ie, in a spherically symmetric manner) - $P = 10^3 W$


Power density $= \frac{P}{4\pi R^2}$ where R = distance from transmitter

We want $\frac{1}{c} \frac{P}{4\pi R^2} = U = 4 \cdot 10^{-14} J/m^3$

$R = \sqrt{\frac{P}{4\pi c U}} = \sqrt{\frac{10^3}{4\pi \cdot 3 \cdot 10^8 \cdot 4 \cdot 10^{-14}}} = \underline{\underline{2580 m}}$ ✓

Q.29

6

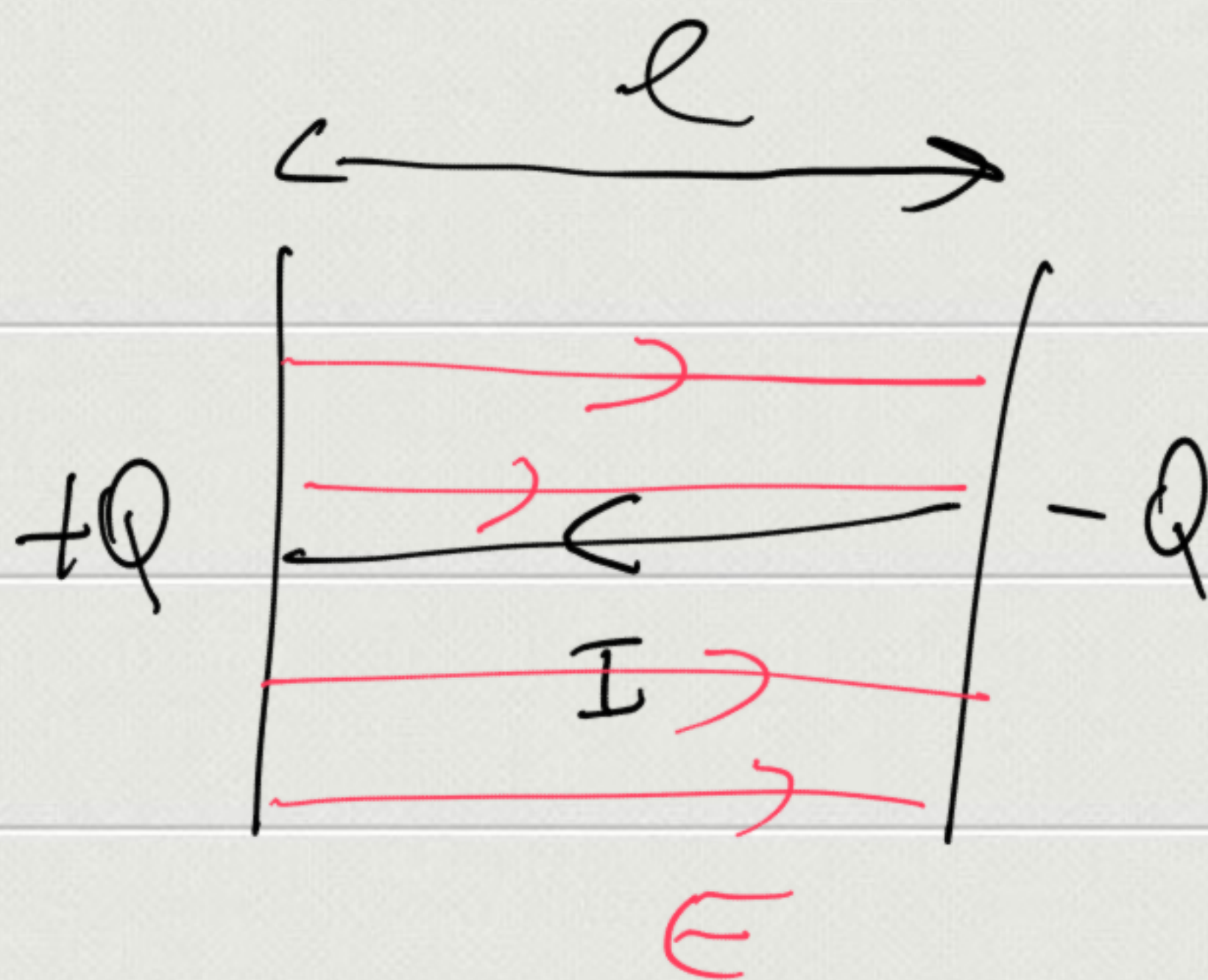

The electric field lines go from one side of the capacitor to the other.

Let A = area of capacitor Q = charge

on capacitor $E = \frac{\sigma}{\epsilon_0} = \frac{Q}{A\epsilon_0}$

Also $\frac{dQ}{dt} = I \Rightarrow I = A\epsilon_0 \frac{dE}{dt}$

Now take a circular path inside the capacitor. Radius r

$$\oint \vec{B} \cdot d\vec{\ell} = 2\pi r B(r)$$

But $\oint \vec{B} \cdot d\vec{\ell} = \mu_0 I - \epsilon_0 \mu_0 \frac{dE}{dt} (\pi r^2)$

(The minus sign is there because I and $\vec{E}$ point in opposite directions, as shown in figure)

$$\Rightarrow B(r) = \frac{\mu_0 I}{2\pi r} - \frac{\epsilon_0 \mu_0 r}{2} \frac{dE}{dt} \left(\frac{A}{\pi r^2} - 1 \right)$$

The Poynting vector is $\vec{S} = \frac{\vec{E} \times \vec{B}}{\mu_0}$

$\vec{S}$ points away from wire.

(7)

The magnitude of S , at a given r

is

$$S = \frac{\epsilon_0}{2} E \frac{dE}{dt} \left(\frac{A}{\pi r} - r \right)$$

The flux of S through a cylinder of radius r and length l is

$$\text{Flux} = S (2\pi r l) = \epsilon_0 E \frac{dE}{dt} l (A - \pi r^2)$$

$$\text{Flux} = \frac{d}{dt} \left[\frac{\epsilon_0 E^2 l (A - \pi r^2)}{2} \right]$$

The energy stored in the cylinder

is

$$U_{\text{cylinder}} = \frac{\epsilon_0 E^2 l \pi r^2}{2}$$

The energy stored in the full capacitor

$$\text{is } U_C = \frac{\epsilon_0 E^2 l A}{2}$$

$$\Rightarrow \frac{\epsilon_0 E^2 l (A - \pi r^2)}{2} \text{ is the}$$

energy stored in the capacitor outside cylinder and its rate of change = flux of pointing vector.